

2.5.9 $A = \begin{pmatrix} -1 & 1 & 0 & 0 \\ -1 & 0 & 1 & 0 \\ 0 & -1 & 1 & 0 \\ -1 & 0 & 0 & 1 \\ 0 & 0 & -1 & 1 \end{pmatrix}$; $A^T = \begin{pmatrix} -1 & -1 & 0 & 0 & -1 & 0 \\ 1 & 0 & -1 & -1 & 0 & 0 \\ 0 & 1 & 1 & 0 & 0 & -1 \\ 0 & 0 & 0 & 1 & 1 & 1 \end{pmatrix}$



$A^T A = \begin{pmatrix} 3 & -1 & -1 & -1 \\ -1 & 3 & -1 & -1 \\ -1 & -1 & 3 & -1 \\ -1 & -1 & -1 & 3 \end{pmatrix}$; $C = \text{diag.}(c_1, c_2, c_3, c_4, c_5, c_6)$

$A^T C A = \begin{pmatrix} c_1+c_2+c_5 & -c_1 & -c_2 & -c_5 \\ -c_1 & c_1+c_2+c_4 & -c_3 & -c_4 \\ -c_2 & -c_3 & c_2+c_3+c_6 & -c_6 \\ -c_5 & -c_4 & -c_6 & c_4+c_5+c_6 \end{pmatrix}$

on row j of $A^T C A$ there will appear the conductances corresponding to the edges connected to ~~edge~~^{node} (j) .

(i.e. node 1: edges (1, 2, 5)
node 2: edges (1, 3, 4)
node 3: edges (2, 3, 6)
node 4: edges (4, 5, 6))

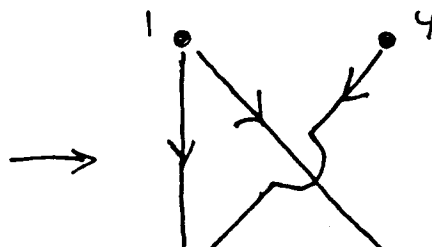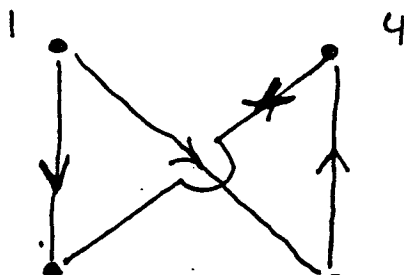2.5.10 if $A = \begin{pmatrix} -1 & 1 & 0 & 0 \\ -1 & 0 & 1 & 0 \\ 0 & 1 & 0 & -1 \\ 0 & 0 & -1 & 1 \end{pmatrix}$ $\rightarrow A' = \begin{pmatrix} -1 & 1 & 0 & 0 \\ -1 & 0 & 1 & 0 \\ 0 & 1 & 0 & -1 \end{pmatrix}$
rows of A' are basis of $\mathcal{R}(A)$.



Spanning tree